
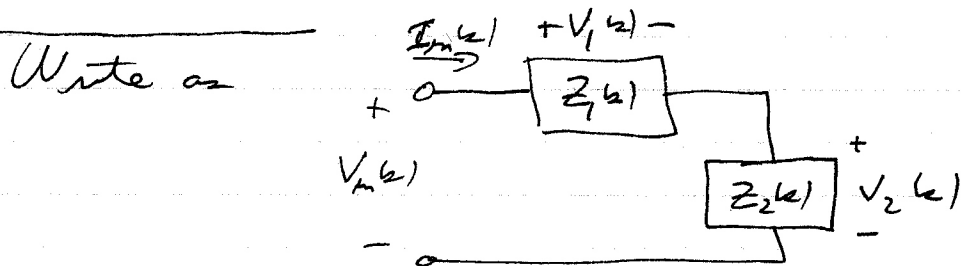


$$z_L = Ls, z_C = \frac{1}{Cs}$$
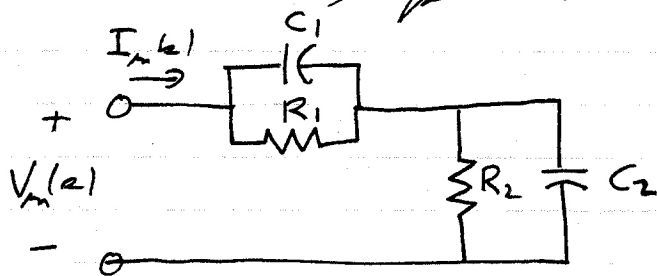
# Recitation of Week 13

① Compute the input impedance,  $z_m(s)$ , of



$$V_m(s) = V_1(s) + V_2(s) = (z_1(s) + z_2(s)) I_m(s)$$

$$\Rightarrow z_m(s) = \frac{V_m(s)}{I_m(s)} = z_1(s) + z_2(s)$$

Since parallel admittances add:

$$z_1(s) = \frac{1}{Y_1(s)} = \frac{1}{C_1 s + \frac{1}{R_1}} = \frac{1/C_1}{s + 1/R_1 C_1}$$


Similarly,

$$z_2(s) = \frac{1/C_2}{s + 1/R_2 C_2}$$

Thus


$$z_m(s) = \frac{1/C_1}{s + 1/R_1 C_1} + \frac{1/C_2}{s + 1/R_2 C_2}$$

② Compute  $v_C(t)$ ,  $t \geq 0$  for

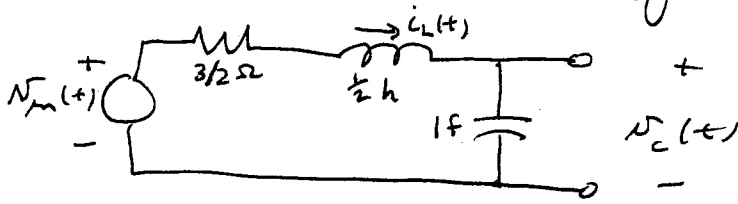


where  $v_m(t) = 10u(t)$ ,  $i_L(0^-) = 2$ ,  $v_C(0^-) =$

Redraw in Laplace domain:

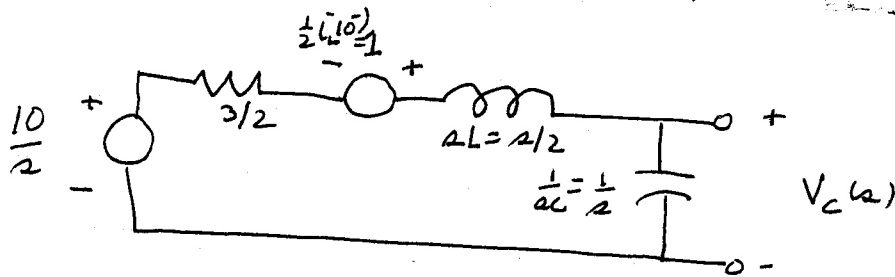

Combine voltage sources:

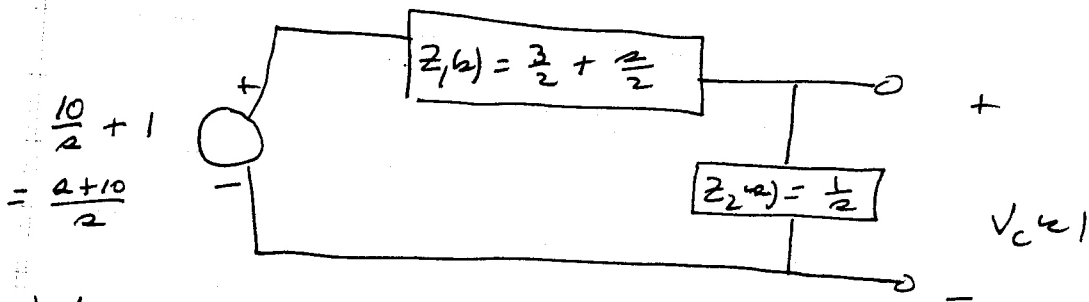

Voltage divider:

$$V_C(s) = \frac{Z_2(s)}{Z_1(s) + Z_2(s)} V_{in}(s) = \frac{1/s}{\frac{4+3}{2} + \frac{1}{2}} \cdot \frac{2+10}{2}$$

$$= \frac{2+10}{2(s^2+3s+2)}$$

--- use PFE at table look up...

$$v_C(t) = K_1 u(t) + K_2 e^{-t} u(t) + K_3 e^{-2t} u(t)$$

③ For a system described by

$$\ddot{y}(t) + \dot{y}(t) = 3x(t) + \dot{x}(t)$$

with  $y(0^-) = 0$ ,  $\dot{y}(0^-) = -1$ ,  $x(t) = e^{-3t} u(t)$   
compute  $y(t)$ .

---

$$\begin{aligned} s^2 Y(s) - s y(0^-) - \dot{y}(0^-) + s Y(s) - y(0^-) \\ = 3 X(s) + s X(s) \end{aligned}$$

$$\Rightarrow (s^2 + s) Y(s) = (s+3) X(s) - 1$$

$$\begin{aligned} X(s) = \frac{1}{s+3} \Rightarrow (s^2 + s) Y(s) &= 0 \\ \Rightarrow Y(s) &= 0 \\ \Rightarrow y(t) &= 0, t \geq 0. \end{aligned}$$

Note: This leads to an interpretation of the zeros of a transfer function!

i.e.

$$H(s) = \frac{s+3}{s(s+1)}$$

for the system above.